

Assignment - 2

- 1) Design a logic circuit whose output is HIGH whenever A & B are both HIGH as long as C & D either both LOW or both HIGH.
- 2) The three switches are used to indicate the status of the door by the driver's seat, the ignition & the headlights respectively. Design the logic circuits with these three switches as inputs so that the alarm will be activated whenever either of the following conditions exists.
- The headlights are ON while the ignition is off.
 - The door is open while the ignition is ON.
- 3) Convert the following into standard SOP
- $Z(A, B, C) = \overline{A}B + BC + \overline{B}\overline{C}$
 - $Z(A, B, C, D) = \overline{A}\overline{B} + \overline{B}\overline{C}D + A\overline{B}\overline{D}$
- 4) Convert the following into standard POS
- $y(A, B, C) = (A + \overline{B})(\overline{B} + \overline{C})C$
 - $y(A, B, C, D) = (\overline{A} + \overline{B} + D)(A + D)(\overline{B} + \overline{C})$
- 5) Convert the following SOP into POS
- $y(A, B, C) = \overline{A}BC + A\overline{B}\overline{C} + BC$
 - $\overline{A}B\overline{C}D + \overline{A}\overline{B}\overline{C} + A\overline{B}D + \overline{A}C\overline{D}$
- 6) Convert the following POS into SOP
- $y(A, B, C) = (\overline{A} + B + C)(\overline{B} + \overline{C})(\overline{A} + C)$
 - $y(A, B, C, D) = (A + \overline{D} + \overline{E})(\overline{B} + C + \overline{D})(\overline{A} + B + D)$
- 7) Simplify the following using K-map method
- 7) $F(P, Q, R, S) = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$
- 8) $F(A, B, C, D) = \sum m(3, 7, 11, 12, 13, 14, 15)$
- 9) $F(P, Q, R, S) = \prod M(3, 5, 7, 8, 10, 11, 12, 13)$
- 10) $F(A, B, C, D) = \prod M(0, 1, 2, 4, 5, 6, 8, 9, 10)$

$$11) f(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + d(0, 2, 14)$$

$$12) f(A, B, C) = \sum m(1, 2, 5, 7) + d(0, 4, 6)$$

$$13) f(A, B, C, D) = \sum m(0, 2, 8, 10, 14) + d(5, 15)$$

$$14) f(A, B, C, D) = \pi M(0, 2, 4, 8, 10, 12) + d(3, 5, 9, 13, 15)$$

$$15) f(A, B, C) = \pi M(0, 5, 7) + d(1, 3, 4)$$

$$16) f(A, B, C) = \pi M(1, 2, 5, 6, 9, 10) + d(11, 12, 13, 14)$$

$$17) F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B + AB\bar{C} + AC$$

$$18) F(A, B, C) = \bar{A}B + B\bar{C} + BC + A\bar{B}\bar{C}$$

$$19) out = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + \bar{A}BCD + AB\bar{C}D + ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

$$20) F(A, B, C) = (A + \bar{B})(\bar{B} + C)(A + B + C)$$

$$21) F(A, B, C, D) = (A + B + C + D)(\bar{A} + \bar{B} + C + D)(\bar{A} + B + \bar{C} + \bar{D})(A + B + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + \bar{D})$$

22)

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1