

Assignment - 3

- 1) Implement the following gates using 2:1 multiplexers
- NOT
 - AND
 - OR
 - NAND
 - NOR
 - EXOR
 - EX-NOR

- 2) Implement Half Adder & Full Adder using MUX
- 3) Implement Half subtractor & Full subtractor using MUX

- 4) Implement the following function with 8:1 MUX
- $$F(A, B, C, D) = \sum m(1, 3, 5, 6, 11, 12) + d(7, 9)$$

- 5) Implement $X = \bar{A}B + ABC + A\bar{C}$ using 4:1 MUX

- 6) Implement the following function by using 4 to 1 MUX and few other gates as possible

$$f(w_1, w_2, w_3, w_4) = \bar{w}_1 \bar{w}_2 \bar{w}_3 \bar{w}_4 + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_2 w_3 w_4$$

Assume that only uncomplemented inputs w_1, w_2, w_3, w_4 are available

- 7) Convert the following flip flop

- SR to T
- JK to SR
- JK to D
- D to T
- T to SR
- T to JK
- T to D

8) Implement 4:16 decoder using 3:8 decoder

9) Implement the following functions using 4:16 decoder

i) $F_1(A, B, C, D) = \sum m(1, 2, 4, 7, 8, 11, 12, 13)$

ii) $F_2(A, B, C, D) = \prod M(10, 12, 13, 14)$

iii) $F_3(A, B, C, D) = \sum m(1, 5, 8, 10)$

10) Implement the following functions using suitable demux & logic gates.

$Y_1 = f_1(A, B, C) = \sum m(0, 1, 3, 5, 6)$

$Y_2 = f_2(A, B, C) = \sum m(0, 1, 2, 4, 6)$

$Y_3 = f_3(A, B, C) = \sum m(1, 2, 3, 6)$ Draw logic diagrams.

11) Implement the following multiple O/P function using suitable Demux.

$f_1(A, B, C) = \sum m(0, 1, 3, 7) + d(2, 5)$

$f_2(A, B, C) = \sum m(1, 5, 7)$

$f_3(A, B, C) = \sum m(0, 2, 4, 6)$

12) Implement 1:16 demux using 1:8 demux